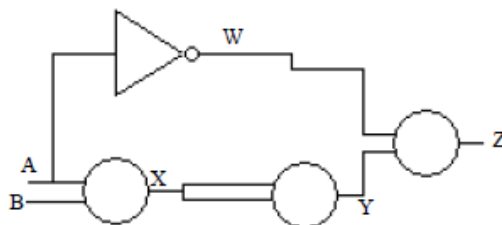


## Logic Gates – Worksheet 3

1. Consider a **truth table** with two inputs **A** and **B**, given that the output **C** is **true** when both inputs are the same.
  - a. Construct the truth table described above.
  - b. Draw the logic circuit for this truth table.
2. James (J), Sue (S) and Mike (M) are three shareholders in a company and they have 650, 300 and 300 shares respectively. Whenever a decision is to be made, they take a vote by pressing a switch in front of them if they are in favour. The vote passes if:
  - i. James alone is in favour
  - ii. Both Sue and Mike are in favour
  - iii. All three are in favour

When the vote passes a bell (B) rings.

- a. Using **J**, **S** and **M** as inputs and **B** as output, draw the **truth table** for the circuit described above. (Assume that logic 1 at an input is a vote in favour and logic 1 at the output implies the bell rings.)
  - b. Draw the **circuit** for the truth table above.
  - c. Write the **Boolean expression** for the circuit in terms of J, S and M.
3. Below is a partly drawn logic circuit and its incomplete truth table.



A	B	W	X	Y	Z
1	0				
0	1		1		
1	1				0
0	0			0	

By examining both the circuit and truth table:

- a. Draw the **circuit again** and replace the three circles with the appropriate logic gates.
- b. Draw and complete the **truth table** to match the circuit.
- c. Write down the **Boolean expression** for this circuit.